


Worksheet 5

Objectives:

- (1) Understand the behavior of Adder circuits.
- (2) Understand the design combinational circuits for different real-world scenarios.

1) Design the following circuit and write the truth tables for them.


(i)

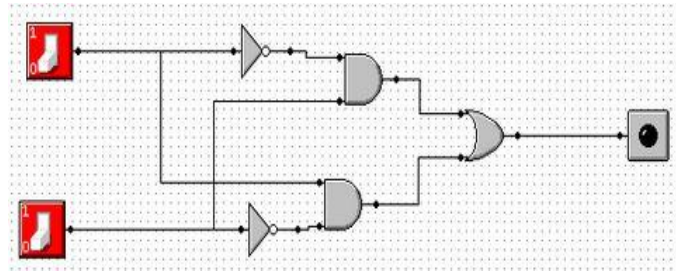

- a) Draw the circuit for A XOR B and write the truth table for them. Identify the similarity between XOR circuit and circuit (i)


(ii)

Half Adder

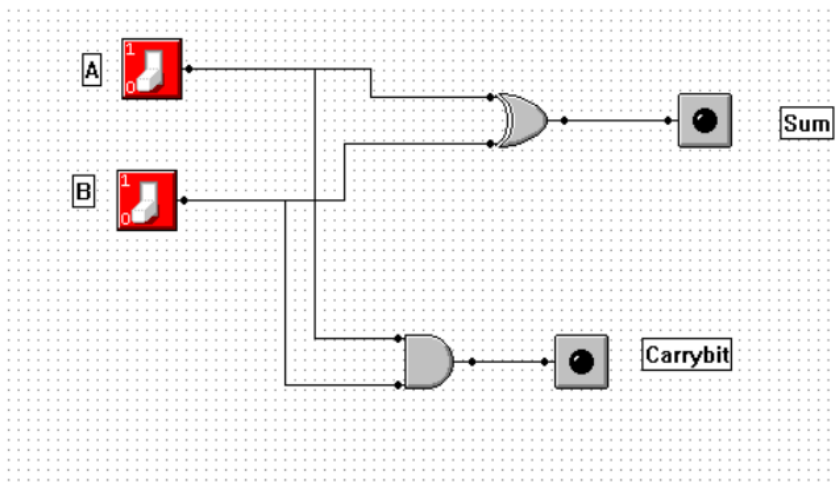

Worksheet 5

(iii)

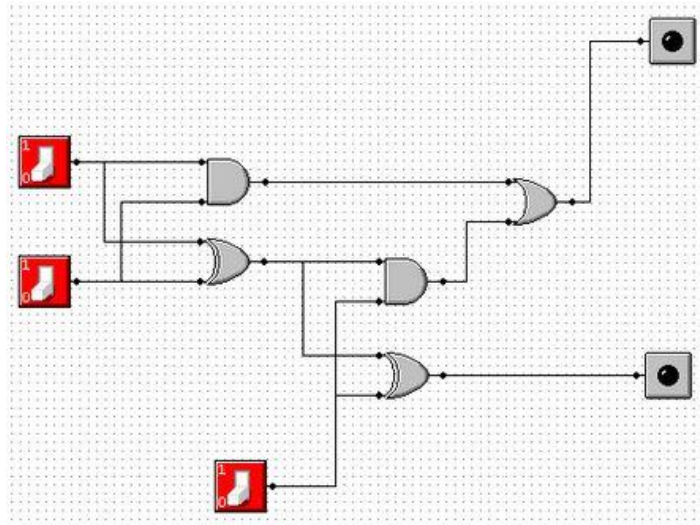Full Adder


Discuss with your friends and lecturer, for what purpose these circuits can be used.

2) Parallel Adder

- a. Modify your Full Adder implementation to conduct addition of two 3-bit binary numbers. The new implementation should give the summation of two numbers and any overflow carry out. You can use the full_adder.lgi that you have drawn in **1)** as the starting point. Save your new files as parallel_adder.lgi


- 3) Binary Decoder:** A binary decoder is a combinational logic circuit that converts binary information from the n coded inputs to a maximum of 2^n unique outputs. They are used in a wide variety of applications, including data demultiplexing, seven segment displays, and memory address decoding. Implement the following decoder circuit in MM Logic and observe its behavior.

Worksheet 5

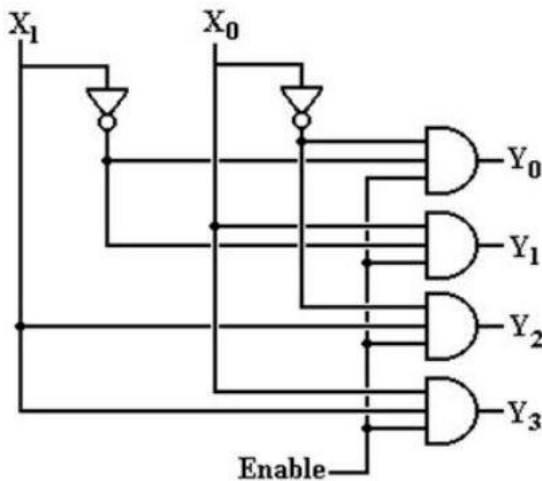

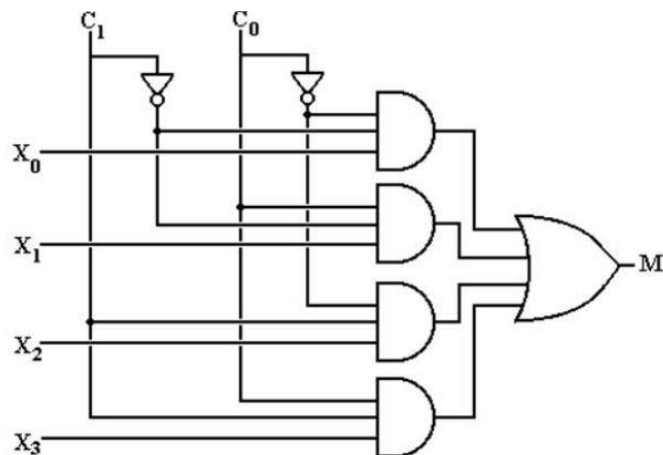
- 4) **Multiplexer:** A multiplexer (or mux) is a device that combines several analog or digital input signals and forwards them into a single output line. A multiplexer of 2^n inputs has n select lines, which are used to select which input line to send to the output.

Implement the following mux circuit in MM Logic and observe its behavior.



- 5) Use 4 to 1 mux and 2 to 4 De-mux available in MM Logic and draw truth tables to recognize their behavior.
- 6) Design the following circuit using MM Logic and observe its behavior using a truth table.

Worksheet 5

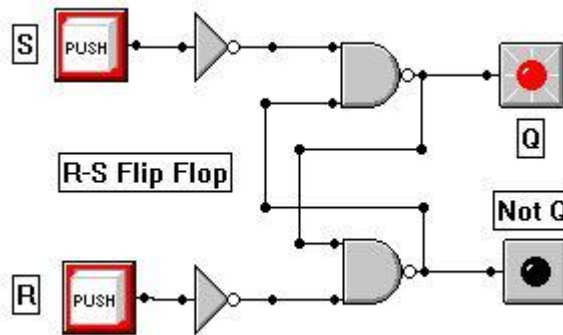

What is the main difference between circuits in 1) – 5) and above circuit.

Activities:

- 7) Learn how to use multiplexer circuits to design decoders and different Boolean functions.

Ex: Use a Mux to implement following Boolean function

$$F = AB\bar{C} + \bar{B}C + AC$$

- 8) Design Circuit to generate the parity bit using even parity scheme for a 3 bit message.

Discuss the steps you need to follow. Design the circuit using MML and verify the output. Save your file as even_parity.lgi.

- 9) Design a circuit to output whether the decimal numbers 0-7(including 0-7), is a prime number or not. Save your file as prime_number.lgi.

- a. If the requirement is only to check decimal numbers 2-7(including 2 and 7), design a new circuit. Save your file as prime_number_2.lgi