



## INTRODUCTION TO COMPUTER SYSTEMS (IT1020)

Year 1, Semester 1


Work Sheet 05

IT22278944, Vikum Chathuranga Basnayaka

Y1.S1.WD.IT.17

11-12-2022


1.

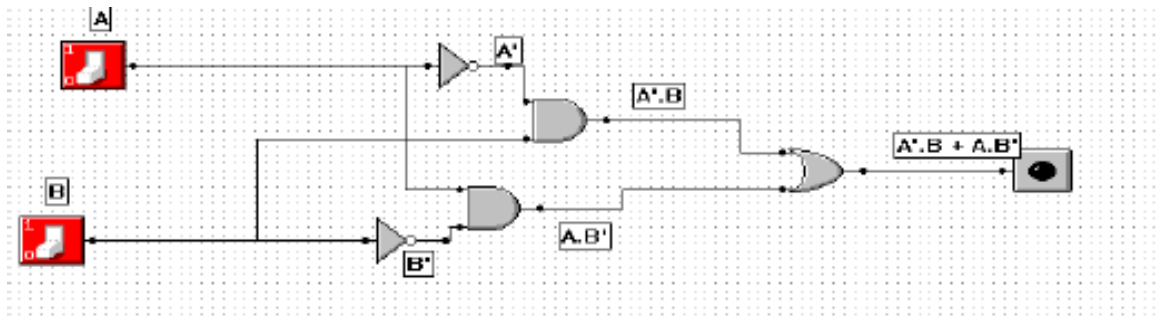

i)

A	B	A'	B'	A'.B	A.B'	F
0	0	1	1	0	0	0
0	0	1	1	0	0	0
0	1	1	0	1	0	1
0	1	1	0	1	0	1
1	0	0	1	0	1	1
1	0	0	1	0	1	1
1	1	0	0	0	0	0
1	1	0	0	0	0	0

a.)

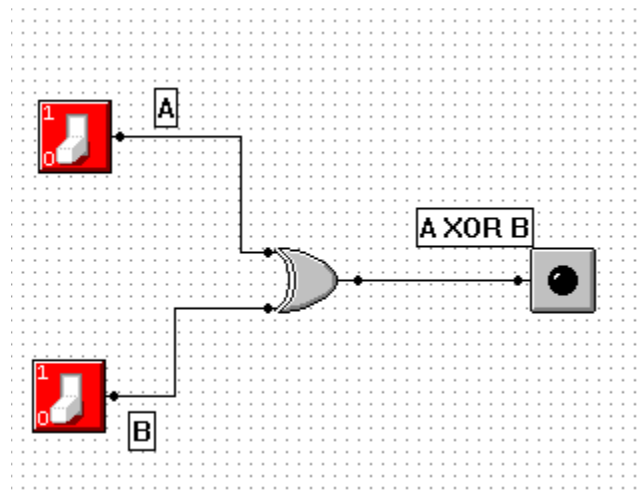


A	B	F
0	0	0
0	1	1
1	0	1
1	1	0

i) The resemblance of the XOR circuit to the circuit


- Light is turned on when one switch is turned on.
- Off when both switches are turned on and off when both switches are turned off.

ii) Half adder

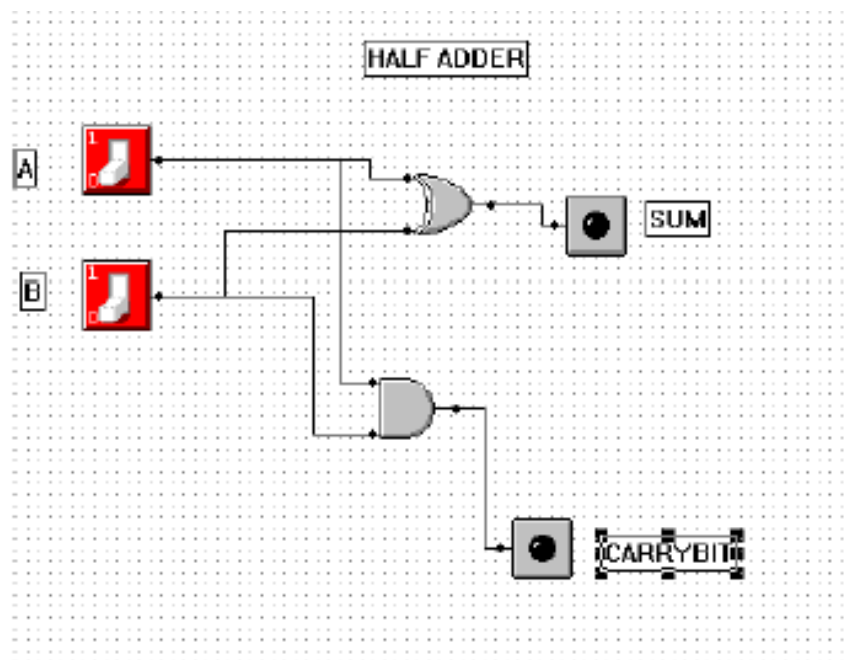

A	B	SUM	CARRYBIT
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

iii) Full adder

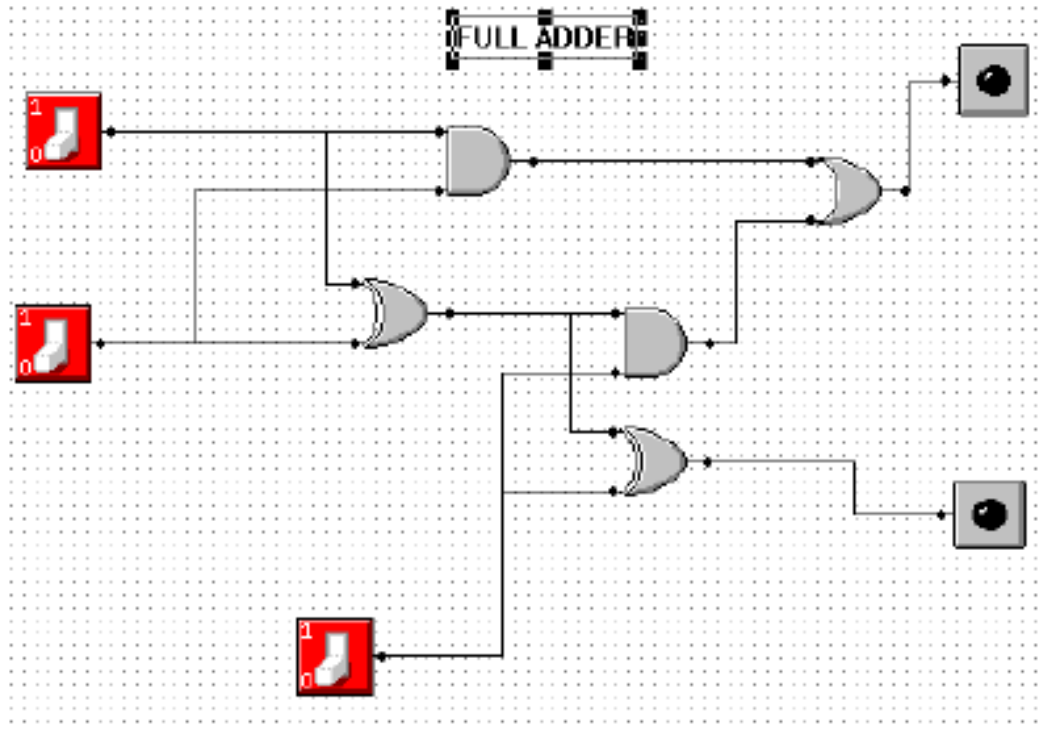


A	B	C	SUM	CARRYBIT
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


The purpose of these circuits is,

- A category of combinational logic circuits known as the Half Adder adds two 1-bit binary digits. It produces the carry as well as the sum of the two inputs. The Full Adder is another a kind of combinational logic that performs addition operations by adding three of the 1-bit binary digits.

## 2. Parallel adder

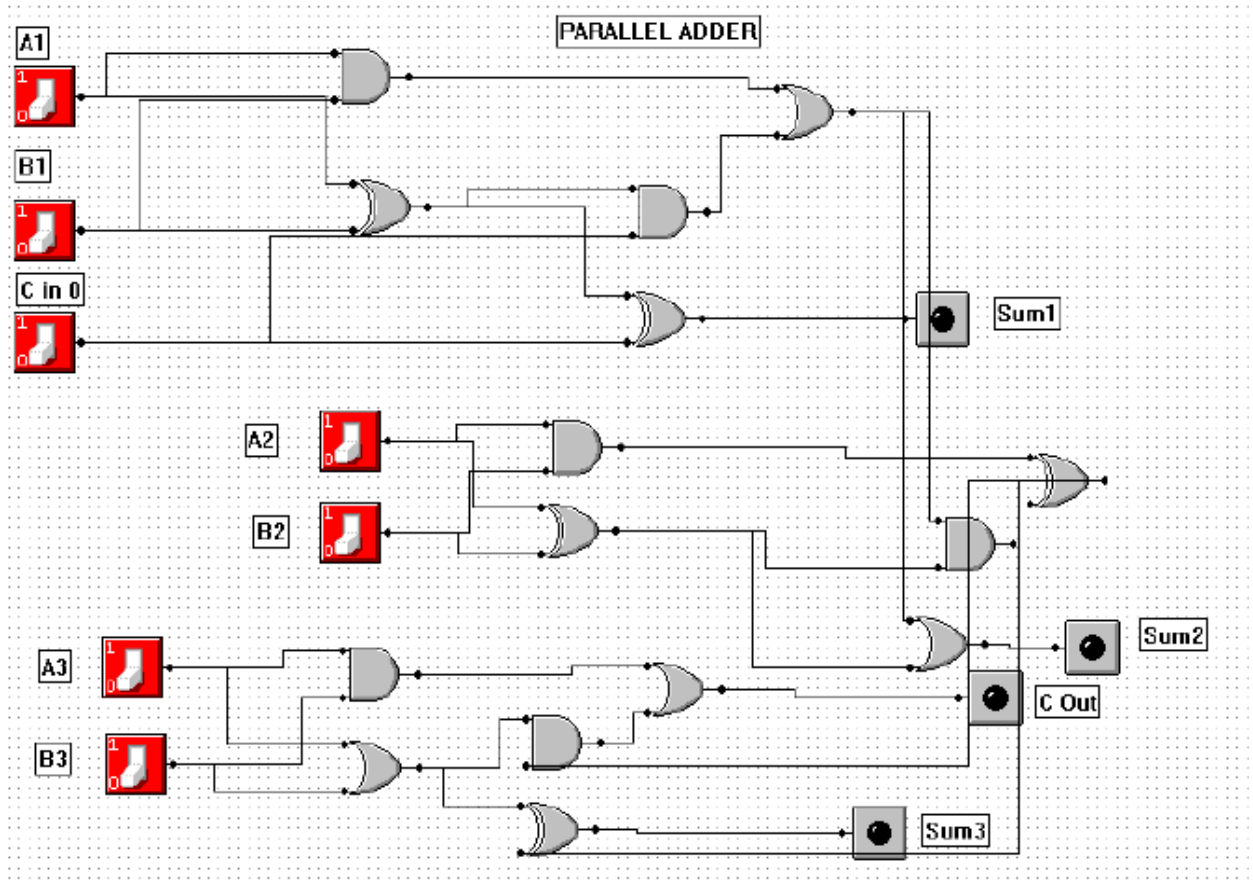


### 3. Binary decoder

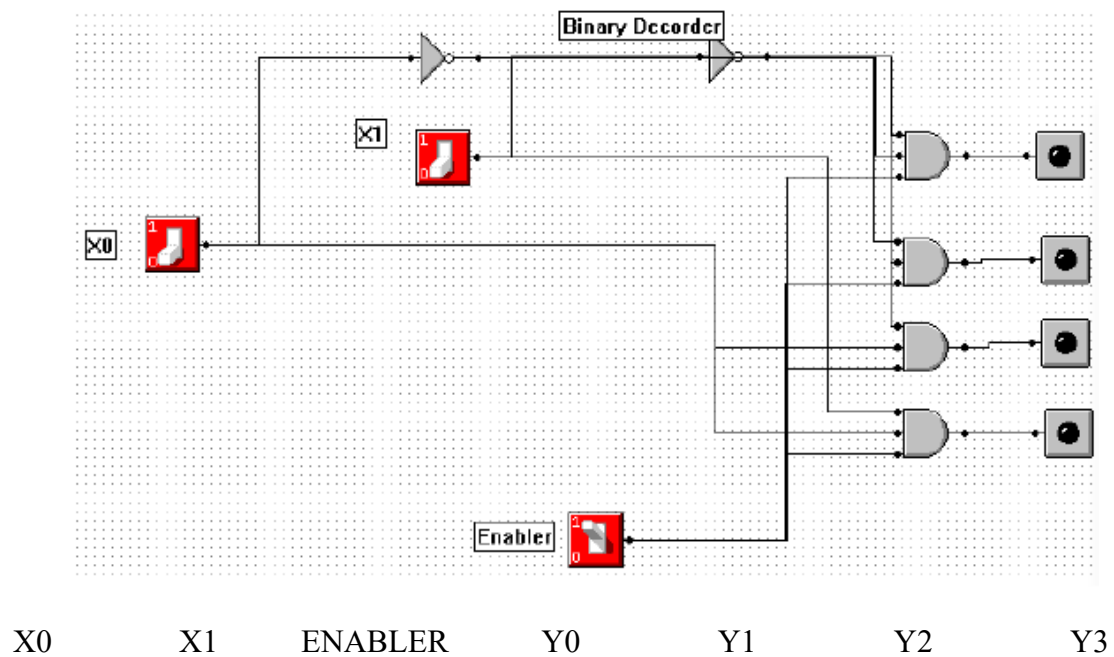


0	0	1	1	0	0	0
0	1	1	0	1	0	0
1	0	1	0	0	1	0
1	1	1	0	0	0	1

#### 4. Multiplexer

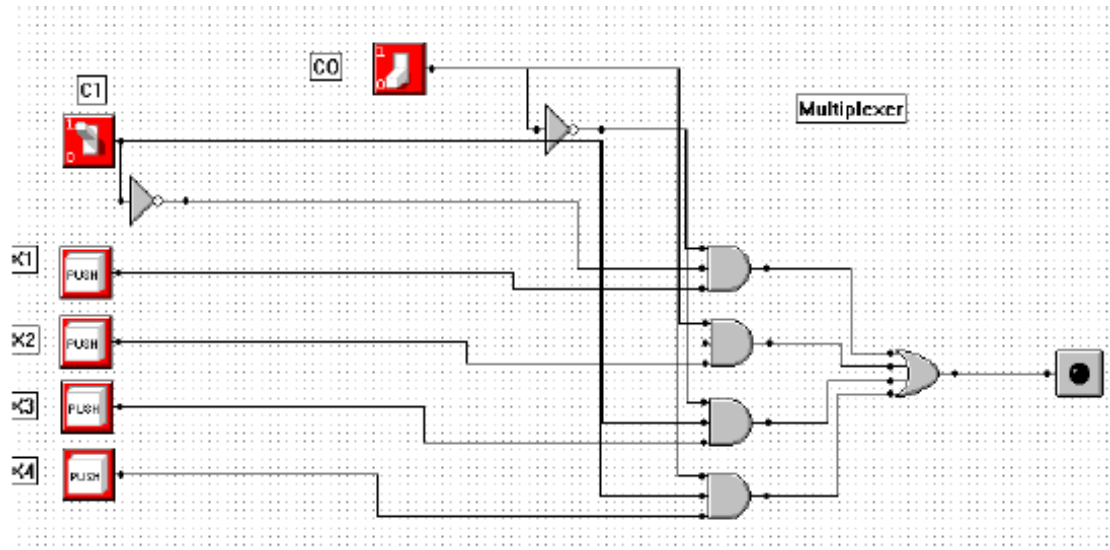


C1	C2	X	M
0	1	0	0
		X1	1
		1	
0	0	0	0
		X2	1
		1	
1	1	0	0
		X3	1
		1	
1	0	0	0
		X4	1
		1	

#### 5. 4 to 1 mux

 


S0	S1	D0	D1	D2	D3	Y
0	0	0	X	X	X	0
0	0	1	X	X	X	1
0	1	X	0	X	X	0
0	1	X	1	X	X	1
1	0	X	X	0	X	0
1	0	X	X	1	X	1
1	1	X	X	X	0	0
1	1	X	X	X	1	1

6. 2 to 1 mux

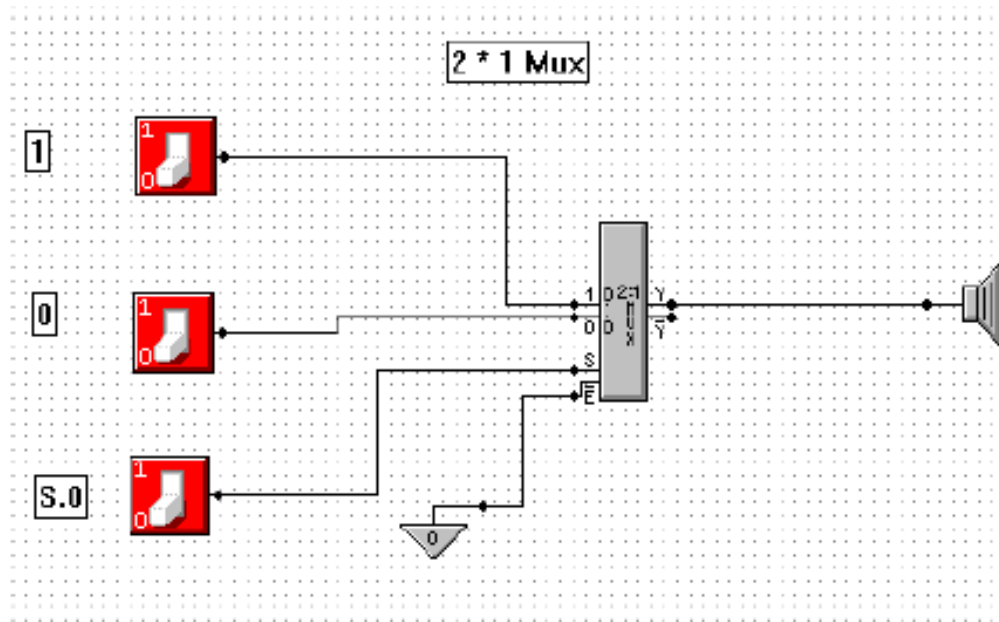

1	0	S0	Y
0	0	X	0
0	1	X	1
1	X	0	0
1	X	1	1

7.  $F = A B C' + B' C + A C$

 


Input			Output
A	B	C	$F = A B C' + B' C + A C$
0	0	0	0



0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

8.

 

9.